


Lec 6: Single Phase AC transformer

Outline of lectures:

- 1] Introduction "Transformer" ^{المحول}
- 2] Mutual Induction ^{الحث المتبادل}
- 3] Transformer construction
- 4] Transformer ratio
- 5] emf equation of a transformer


I] Transformer

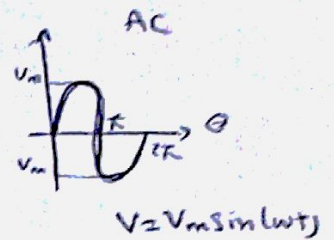AC: Alternating current ^{التيار المتغير (المتكرر)}




Single Phase (220V, 50Hz) ^{آحادى البوصلة}

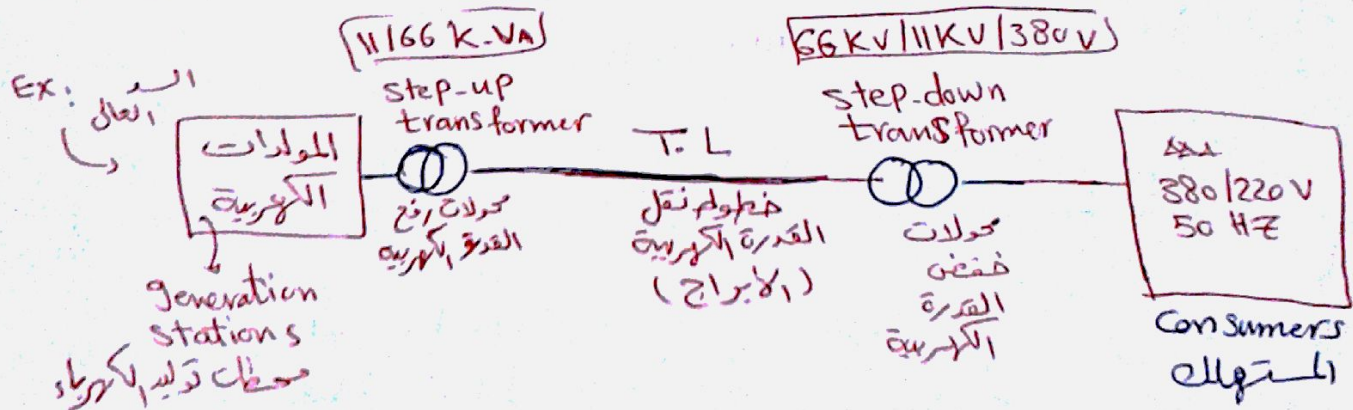Three phase (380/220V, 50Hz) ^{ثلاثى البوصلة}



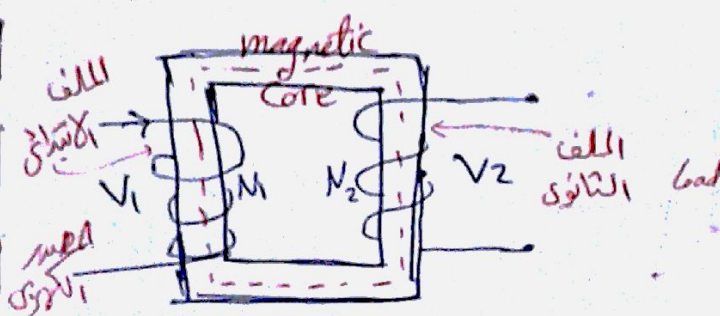Transformer ^{ثابت} [static Machine] \Rightarrow Mechanical losses = 0



$$e.m.f = N \frac{d\phi}{dt}$$

عدد اللفات

* يتكون المحول من ملفين من النحاس (ملف ابتدائي، ملف ثانوي) وقلب من الحديد

* يتغير المصدر (V_1) \Rightarrow فينتج (ϕ) ويتولد V_2 (دفع في (emf))

② Mutual Inductance

حث متبادل

- * By Varying I_1 as induced emf associated with the changing in magnetic flux in coil ②

$$E_{21} = -N_2 \frac{d\phi_{21}}{dt}$$

$$N_2 \frac{d\phi_{21}}{dt} \propto \frac{dI_1}{dt}$$

$$\therefore N_2 \frac{d\phi_{21}}{dt} = M_{21} \frac{dI_1}{dt}$$


M_{21} = Mutual inductance between coil ① & coil ②

Also, in a similar manner

$$E_{12} = -N_1 \frac{d\phi_{12}}{dt}, \quad N_1 \frac{d\phi_{12}}{dt} = M_{12} \frac{dI_2}{dt}$$



$M_{12} = M_{21} = M$ = Mutual induction

الحث المتبادل

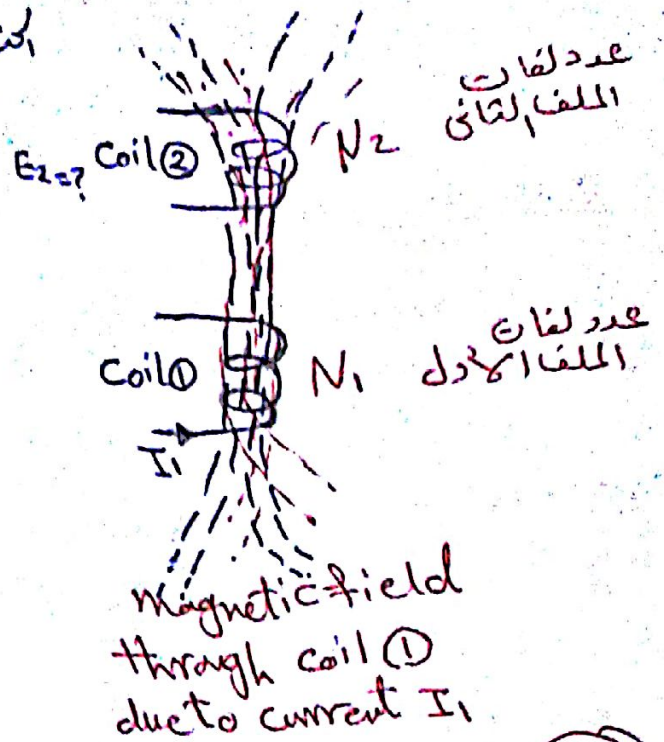

فكرة عمل المولد هي الحث المتبادل

Transformer Construction

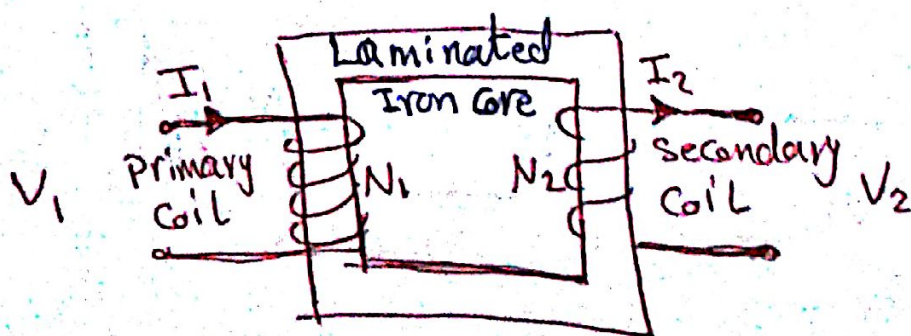
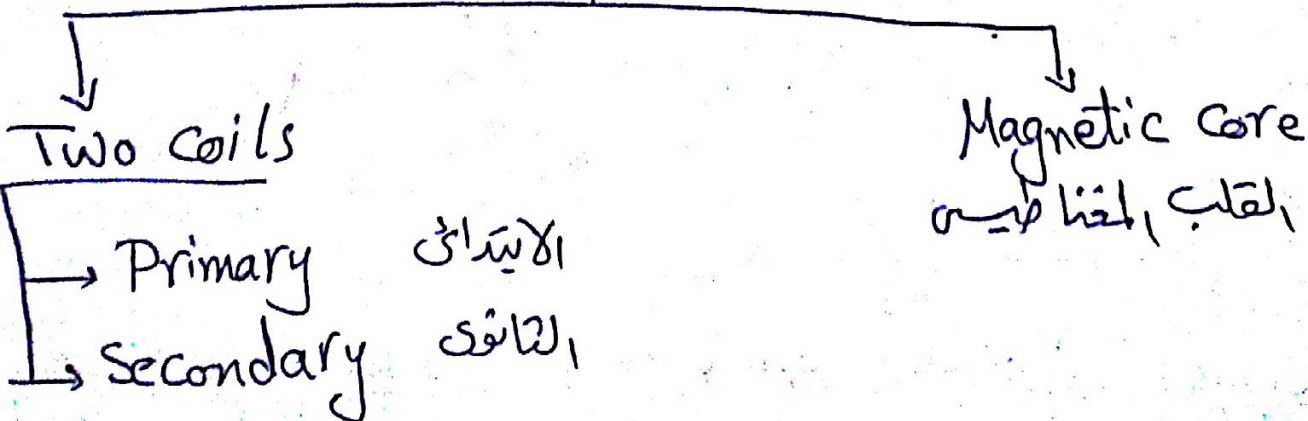


- " A transformer is an electric device, using the phenomenon of mutual inductance to transfer electric energy from one circuit to another circuit "

Types of transformer

Shell type

Core type

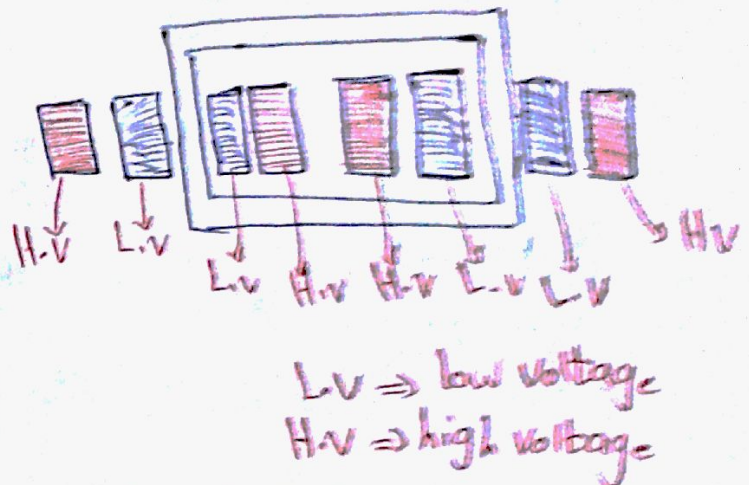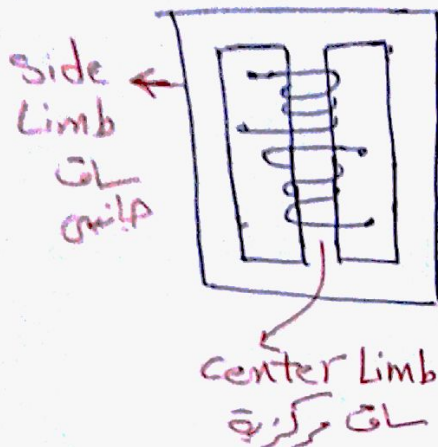

فائزال : State the types of AC transformer and compare between them?
 الأنواع المختلفة من المحولات وكيفية عملها

- Transformation ratio $\frac{E_1}{E_2} = \frac{N_1}{N_2}$

$$\boxed{\frac{E_1}{E_2} = \frac{N_1}{N_2}}$$

E_1 = induced emf on Primary coil

N_1 = No. of turns of Primary coil

E_2 = induced emf on secondary coil

N_2 = No. of turns of secondary coil


No copper losses ($\neq 0$)

$$V_1 = E_1, V_2 = E_2$$

$$\boxed{\frac{E_1}{E_2} = \frac{V_1}{V_2} = \frac{N_1}{N_2}}$$

V_1 → source voltage

V_2 → load voltage

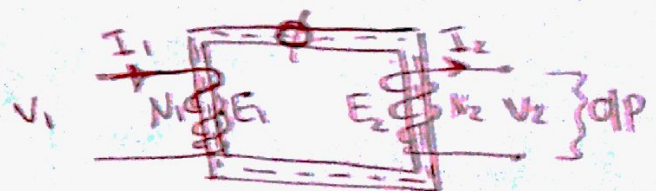

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\boxed{V_2 = \frac{N_2}{N_1} V_1}$$

if $N_2 > N_1 \Rightarrow V_2 > V_1 \Rightarrow$ (step-up transformer)

if $N_2 < N_1 \Rightarrow V_2 < V_1 \Rightarrow$ (step-down transformer)

emf equation of a transformer

Prove that: $E = 4.44 f N \phi_m$

where: (E) is the induced voltage

(f) is the frequency

(N) is the Number of turns

(ϕ_m) is the max. flux density

$$\text{Let } \phi = \phi_m \sin \omega t$$

$$E_1 = - \frac{N d\phi}{dt} = - N \frac{d(\phi_m \sin \omega t)}{dt}$$

$$E_1 = - N \phi_m \frac{d \sin \omega t}{dt} = \boxed{- N \phi_m \omega \cos \omega t}$$

$$\therefore \boxed{E_1 = N \phi_m \omega \sin \left(\omega t - \frac{\pi}{2} \right)}$$

$$\text{At } \boxed{\cos(30^\circ) = -\sin(60^\circ) = -\sin(30^\circ - 90^\circ)}$$

$$\omega = 2\pi f$$

$$\therefore E_1 = 2\pi f N \phi_m \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$E_1 = E_{1 \text{ max}} \cdot \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$E_{1 \text{ max}} = 2\pi f N \phi_m$$

$$\therefore E_{1 \text{ rms}} = \frac{E_{1 \text{ max}}}{\sqrt{2}} = 4.44 f N \phi_m$$

\therefore rms value of

$$\begin{aligned} & \left. \begin{aligned} E_1 &= 4.44 f N_1 \phi_m \\ E_2 &= 4.44 f N_2 \phi_m \end{aligned} \right\} E_1/E_2 = N_1/N_2 \end{aligned}$$

$$\text{or } \boxed{V = V_m \sin \omega t}$$